



K22P 1591

Reg. No. : .....

Name : .....

**I Semester M.Sc. Degree (CBSS – Reg./Sup./Imp.) Examination, October 2022**  
**(2019 Admission Onwards)**  
**PHYSICS**

**PHY – 1C04 : Electronics**

Time : 3 Hours

Max. Marks : 60

**SECTION – A**

Answer both questions either (a or b from each question).

(2×12=24)

1. a) Deduce the expression for the closed loop voltage gain, Input resistance, output resistance and band width of a voltage series feedback amplifier using Op-Amp. How will you construct an amplifier of minimum gain, in voltage series feedback configuration ?

OR

- b) Explain the working of first order low pass and high pass Butterworth filters. Also draw the frequency response and explain it's behaviour.

2. a) What is meant by D/A converter ? What are the parameters used to define the performance of D/A converter ? With the help of a diagram explain the working of R-2R ladder network type DAC.

OR

- b) With the help of a functional block diagram explain the internal architecture and register array of Intel 8085 microprocessor.

**SECTION – B**

Answer any 4. (1 mark for Section a, 3 marks for Section b and 5 marks for Section c).

(4×9=36)

3. a) What is a shift register ?  
 b) What are the various types of shift registers used ?  
 c) Draw the logic diagram and symbol of an 8-bit serial-in-parallel-out shift register and explain it's working.

P.T.O.

K22P 1591



4. a) What is a summing amplifier ?  
 b) Explain how an Op-Amp works as a summing amplifier and derive the expression for the output of a summing amplifier.  
 c) What is the output voltage of an Op-Amp inverting summing amplifier for the following set of input voltages and resistors  $R_f = 1 \text{ M}\Omega$  in all cases,  $V_1 = +1 \text{ V}$ ,  $V_2 = +2 \text{ V}$ ,  $V_3 = +3 \text{ V}$ ,  $R_1 = 500 \text{ k}\Omega$ ,  $R_2 = 1 \text{ M}\Omega$ ,  $R_3 = 1 \text{ M}\Omega$ . ?  
 What would be the expression for the output voltage if you replace  $R_f$  with a capacitor C ?
5. a) What are synchronous counters ?  
 b) Discuss its advantage over asynchronous counter.  
 c) Draw the timing diagram of a 4 bit synchronous up-counter and explain.
6. a) What is the function of differentiator a circuits ?  
 b) Show that an Op-Amp differentiator circuit performs the differentiation operation.  
 c) Design a differentiator circuit to differentiate an input signal that varies from 10 Hz to 2 kHz. Assume  $C_1 = 0.1 \text{ }\mu\text{F}$ .
7. a) What is an astable multivibrator ?  
 b) Explain the construction of Astable multivibrator using 555 timer.  
 c) Calculate the frequency and duty cycle of 555 Astable multivibrator given  $C = 0.01 \text{ }\mu\text{F}$ ,  $R_A = 10 \text{ K}\Omega$ , and  $R_B = 50 \text{ K}\Omega$ . Also draw the output waveform.
8. a) What is meant by ROM ?  
 b) Draw the block diagram of a typical ROM and explain.  
 c) Discuss five applications of ROM.