



Reg. No. : .....

Name : .....



K18U 0510

II Semester B.Sc. Degree (CBCSS-Reg./Supple./Imp.)  
Examination, May 2018  
CORE COURSE IN PHYSICS  
2B02 PHY : Electronics – I  
(2014 Admn. Onwards)

Time : 3 Hours

Max. Marks : 40

*Instruction : Write answers in English only.*

SECTION – A

(Answer **all**-Very short answer type-**Each** question carries **one** mark.)

1. The point of intersection of dc and ac load line represents \_\_\_\_\_
2. A JFET is a \_\_\_\_\_ driven device.
3. The 8 bit binary equivalent of  $(187)_{10}$  is \_\_\_\_\_
4. NAND gate is known as \_\_\_\_\_ gate. (4×1=4)

SECTION – B

(Answer **any seven**-Short answer type-**Each** question carries **two** marks.)

5. Common collector circuit is known as emitter follower. Comment on it.
6. What is stabilization of operating point ? What is its need ?
7. Define  $\alpha$ . Show that  $\alpha$  is always less than unity.
8. Why JFET is known as unipolar transistor ?
9. List any four advantages of JFET.

P.T.O.




10. Define the following terms

- i) Shorted gate drain current
- ii) Pinch off voltage.

11. What are the three basic logic gates ?

 12. What is the Boolean equation for the output of figure below ? What is the output if one input is high ?



13. Convert the decimal number 46 into binary equivalent.

14. Explain the signed magnitude scheme with an example.

(7×2=14)

### SECTION – C

(Answer **any four**-short essay/problem type-**Each** question carries **three** marks.)

15. The collector leakage current in a transistor is  $250 \mu\text{A}$  in CE arrangement. If the transistor is connected in CB arrangement, what will be the leakage current.

16. In a Common Base connection  $\alpha = 0.95$ . The voltage drop across  $2\text{k}\Omega$  resistance which is connected in the collector is  $2\text{V}$ . Find the base current.

17. What are the JFET parameters ? Obtain a relation between them.

18. In an n-channel JFET biased by potential divider method, it is desired to set the operating point at  $I_D = 2.5 \text{ mA}$  and  $V_{DS} = +8 \text{ V}$ . If  $V_{DD} = 30\text{V}$ ,  $R_1 = 1\text{M}\Omega$  and  $R_2 = 500 \text{ K}\Omega$ . Find the values of  $R_s$ . The parameters of JFET are  $I_{DSS} = 10\text{MA}$  and  $V_{GS}(\text{off}) = -5\text{V}$ .

19. State and prove de-Morgan's theorem.

20. Subtract 7 from 18 by two's complement method.

(4×3=12)

### SECTION – D

(Answer **any two**-Long essay type-**Each** question carries **five** marks.)

21. Describe the potential divider method in detail. Derive an expression for stability factor.

22. Explain the construction and working of a JFET.

23. Explain combinational logic circuits using NAND and NOR gates.

24. What are binary coded decimals ? How two BCD numbers are arithmetically operated ?  
(2×5=10)