



K19U 0274

Reg. No. : .....

Name : .....

II Semester B.Sc. Degree (CBCSS – Reg./Supple./Improv.)  
Examination, April 2019  
(2014 Admission Onwards)  
CORE COURSE IN PHYSICS  
2B02 PHY : Electronics – I

Time : 3 Hours

Max. Marks : 40

*Instruction : Write answers in English only.*

SECTION – A

Answer **all** – Very short answer type – **Each** question carries **one** mark.

1. The parameter which controls the JFET is \_\_\_\_\_ voltage.
2.  $(11001)_2 =$  \_\_\_\_\_
3. The phase difference between the input and output voltages of a transistor connected in common emitter arrangement is \_\_\_\_\_
4. \_\_\_\_\_ is a universal gate.

SECTION – B


Answer **any seven** – Short answer type – **Each** question carries **two** marks.

5. What are the essentials of a transistor biasing circuit ?
6. What are the different types of biasing used in transistors ?
7. Derive the relation between  $\alpha$  and  $\beta$ .
8. Compare BJT and JFET.

P.T.O.



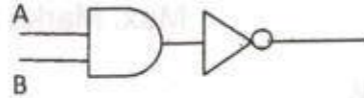9. Explain the working of XOR gate with a circuit diagram.
10. Why a JFET has high input impedance ?
11. Convert the decimal number 133 into binary equivalent.
12. What is positional number system ?
13. What is the Boolean equation for the output of figure below ? What is the output if one of the inputs is high ?



14. Explain signed numbers.

## SECTION – C

Answer **any four** – Short essay/problem type – **Each** question carries **three** marks.

15. The collector leakage current in a transistor is  $250 \mu\text{A}$  in CE arrangement. If the transistor is connected in CB arrangement, what will be the leakage current ?
16. What are the JFET parameters ? Obtain a relation between them.
17. A JFET has a drain current of  $5 \text{ mA}$ . If  $I_{\text{DSS}} = 10 \text{ mA}$  and  $V_{\text{GS}} (\text{Off}) = -6\text{V}$ , find the value of  $V_{\text{GS}}$  and  $V_{\text{P}}$ .
18. For a single stage transistor amplifier, the collector load  $R_{\text{C}} = 2\text{K}\Omega$  and  $i/p$  resistance  $R_{\text{i}} = 1\text{K}\Omega$ . If the current gain is 50, calculate the voltage gain of the amplifier.
19. Which are the basic logic gates ? Explain them with proper diagram and truth table.
20. Convert decimal 65535 to its hexadecimal and hexadecimal to binary equivalents.



## SECTION – D

Answer **any two** – Long essay type – **Each** question carries **five** marks.

21. Explain the CE characteristics of a transistor. Draw input and output characteristics.
22. Explain the construction and working of a JFET.
23. Explain universal gates with proper diagram and truth table. Also prove de-Morgan's theorem.
24. Write short notes on :
  - i) Binary numbers.
  - ii) Hexadecimal numbers.
  - iii) Octal numbers.