



## SECTION - D

Answer **any one** question. Weightage 4 :

29. Describe the construction and working of
- Differentiator
  - Integrator.
- What are their applications ?
30. Explain the concept of power amplification. Draw the circuit of a class A power amplifier and explain how it works. Determine the voltage gain, output power and efficiency. **(1×4W=4 W)**



Reg. No. : .....

Name : .....

**V Semester B.Sc. Degree (CCSS-Reg./Supple./Imp.)**  
**Examination, November 2014**  
**(2012 Admn.)**  
**CORE COURSE IN PHYSICS**  
**5B09 PHY : Basic Electronics**

Time : 3 Hours

Max. Weightage : 30

## SECTION - A

Answer **all** questions :

- If the input coupling capacitor is open, the AC input voltage will
  - Decrease
  - Increase
  - Be zero
  - None of these
- The maximum efficiency of a push-pull amplifier is
  - 25%
  - 50%
  - 78.5%
  - 90%
- At the unity-gain frequency the open loop voltage gain is
  - Zero
  - Infinity
  - One
  - Avmd
- A transistor acts like a diode and
  - Voltage source
  - Current source
  - Resistance
  - Power supply
- The pinch off voltage has the same magnitude as the
  - Gate voltage
  - Gate source voltage
  - Gate source cut off voltage
  - Drain source voltage



6. The base of an npn transistor is thin and
- Metallic
  - Heavily doped
  - Lightly doped
  - Insulated
7. The Hartley oscillator uses
- Negative feedback
  - Two inductors
  - A tickler coil
  - Tungsten lamp
8. A summing amplifier can have
- No more than two input signals
  - Two or more input signals
  - A closed loop input impedance of infinity
  - Small open loop voltage gain

(2×1W=2 W)

## SECTION – B

Answer **any six** questions. Weightage **1 each** :

- Draw the output characteristics of an NPN transistor in CE configuration. Define beta of transistor.
- What is Quiescent point ? Show graphically.
- Define slew rate of an opamp. What is the slew rate of opamp 741C ?
- Define CMMR of an opamp. What is its value in the case of an ideal opamp ?
- Explain the Barkhausen criteria for oscillations.
- What is miller effect ? How does it affect the gain of a CE amplifier ?
- Compare the different amplifier configurations.
- How does gate voltage control drain current in a JFET ?

(6×1W=6 W)



## SECTION – C

Answer **any nine** questions. Weightage **2 each**

- Explain the difference between dc and ac voltage followers.
- What is a non inverting amplifier ? 741 C is connected as a non inverting amplifier for a gain of 100. Determine the stability of the amplifier at this gain.
- Explain the voltage divider bias method of biasing a transistor. Why is it a popular bias circuit ?
- Draw the ac equivalent circuit of a CE amplifier and obtain an expression for the voltage gain.
- Explain the principle of feedback amplifiers. Compare positive feedback and negative feedback.
- What are the advantages of negative feedback ? An amplifier has an open loop gain of 400 and a feedback factor of 0.2. Find the percentage change in closed loop gain if the open loop gain changes by 25%.
- Explain an integrating circuit. What are their uses ?
- Explain Gate bias and Self bias method of FET biasing.
- For a N channel JFET,  $I_{DSS} = 8.7\text{mA}$ ,  $V_p = -3\text{V}$ ,  $V_{GS} = -1\text{V}$ . Find the values of
  - $I_D$
  - $g_{mo}$
  - $g_m$
- Draw the transfer characteristic of JFET. For a JFET,  $I_{DSS} = 16\text{mA}$  and  $V_{GS(off)} = -5\text{V}$ . Determine the drain current  $I_D$  for  $V_{GS} = 0\text{V}$ ,  $-1\text{V}$ , and  $-4\text{V}$
- In a negative feedback amplifier,  $A = 100$ ,  $B = 0.04$  and  $V_i = 50\text{mV}$ . Find
  - Gain with feedback
  - Output voltage
  - Feedback factor
  - Feedback voltage
- Explain the principle of working of a differential amplifier. Define CMRR. What is its value for an ideal opamp ?

(9×2W=18 W)