



M 9909



Reg. No. :

Name :

V Semester B.A./B.Sc./B.Com./B.B.A./B.B.A.T.T.M/B.B.A.R.T.M./B.B.M./
B.C.A./B.S.W./B.A. Afsal-UI-Ulama Degree (CCSS-Reg./Supple./Imp.)
Examination, November 2015
OPEN COURSE
5D01PHY (B) : Applied Electronics

Time: 2 Hours

Max. Weightage : 20

SECTION - A

Answer all questions :

1. With the same secondary voltage and filter which has the most ripple ?
 - a) Half wave rectifier
 - b) Bridge rectifier
 - c) Full wave rectifier
 - d) Clamper
2. If the collector resistor is open, the collector voltage is
 - a) Low
 - b) High
 - c) Unchanged
 - d) Infinite
3. In a loaded zener regulator which is the largest current
 - a) Series current
 - b) Zener current
 - c) Load current
 - d) None of these
4. To reduce the distortion of an amplified signal you can increase the
 - a) Collector resistance
 - b) Emitter feedback resistance
 - c) Generator resistance
 - d) Load resistance
5. The transconductance curve is
 - a) Linear
 - b) Non linear
 - c) Like the graph of a resistor
 - d) Like a single drain curve

P.T.O.



6. In a differential amplifier, a common mode signal is applied to
- a) The non inverting input b) The inverting input
c) Both inputs d) Top of the tail resistor
7. The voltage gain of an Opamp is unity at the
- a) Cutoff frequency b) Unity gain frequency
c) Generator frequency d) Power bandwidth
8. How many NOR gates are required to obtain AND operation
- a) 2 b) 3
c) 4 d) 1

(2×1W=2W)

SECTION – B

Answer **any six** questions :

9. What are the elements of Radiobroadcasting ?
10. Calculate the effective value when three resistances are connected in series.
11. Calculate the effective value when three resistances are connected in parallel.
12. What is a tuned circuit ? Where is it used ?
13. What is a bandpass filter ?
14. What is an ideal diode ?
15. What is an SCR ? Give its application.
16. What is ripple ? How can it be reduced ?
17. What is an op-amp ? Give its uses.
18. What is time constant ? Give the time constant of an LR circuit.

(6×1W=6W)

SECTION – C

Answer **any four** questions :

19. Calculate the effective capacitance when capacitors are connected in
- a) Parallel
b) Series.



20. What are active filters ? Explain the working of a Low pass filter.
21. What is a high pass filter ? How is it designed ?
22. Explain the effects of negative feedback in amplifiers ? What is its advantage ?
23. Explain the principle of working of an oscillator.
24. How are NAND gates constructed ? Give the truth table.
25. What are binary numbers ? How is decimal to conversion done ?
26. What is a signal generator ? Mention their uses.

(4×2W=8W)

SECTION – D

Answer **any one** question.

27. Using circuit describe the construction and working of a full wave rectifier. What is the effect of an RC filter on the output voltage.
28. Explain the working of a digital to analog converter. Determine the resolution of a 12 bit DAC.

(1×4W=4W)