

21. What is a high pass filter? How is it designed?
 22. Explain zener action. How is a voltage regulator constructed using a zener diode?
 23. Explain the principle of working of an oscillator.
 24. What are inverting amplifiers? Explain its working using an op-amp.
 25. What are binary numbers? How is decimal to conversion done?
 26. Explain the working of an analog multimeter.

SECTION - D

27. Using circuit describe the construction and working of a full wave rectifier. What is the effect of an FRC filter on the output voltage?
 28. Explain the working of a digital to analog converter. Determine the resolution of a 8 bit DAC.



Reg. No. :

Name :

**V Semester B.A./B.Sc./B.Com./B.B.A./B.B.A.T.T.M./B.B.M./B.C.A./B.S.W./
 B.A. Afsal-UI-Ulama Degree (CCSS-Reg./Supple./Imp.)
 Examination, November 2014
 OPEN COURSE
 5D01 PHY(B) : Applied Electronics**

Time : 2 Hours

Max. Weightage : 20

SECTION - A

Answer all questions :

- With the same secondary voltage and filter which has the most ripple ?
 a) half wave rectifier b) bridge rectifier
 c) full wave rectifier d) clamper
- What is the PIV across each diode of a bridge rectifier with a secondary voltage of 20 V rms ?
 a) 14.1 V b) 20 V c) 28.3 V d) 6.37 V
- In a loaded zener regulator which is the largest current ?
 a) series current b) zener current
 c) load current d) none of these
- The voltage divider bias has a stable Q point like
 a) base bias b) emitter bias
 c) collector feedback bias d) Emitter-feedback bias
- The transconductance curve is
 a) Linear b) Non Linear
 c) Like the graph of a resistor d) Like a single drain curve
- An SCR is turned on by
 a) Break over b) Gate trigger c) Break down d) Holding current



7. The voltage gain of an Opamp is unity at the
- | | |
|------------------------|-------------------------|
| a) cutoff frequency | b) unity gain frequency |
| c) generator frequency | d) power bandwidth |
8. A combinational circuit can be designed using only
- | | |
|--------------|-----------------------|
| a) AND gates | b) OR gates |
| c) NOR gates | d) OR and X-NOR gates |

(W= 2×1=2)

SECTION – B

Answer **any six** questions :

9. What are the elements of Radio broadcasting ?
10. What are passive elements and active elements ?
11. Calculate the effective value when three resistances are connected in parallel.
12. What is self inductance ?
13. What is a bandpass filter ?
14. How does an LED emit light ?
15. What is an SCR ? Give its application.
16. What property of the transistor is made use of to work it as a switch ?
17. What is an op-amp ? Give its uses.
18. Draw an OR gate. Give its truth table.

(W=6×1=6)

SECTION – C

Answer **any four** questions :

19. Calculate the effective capacitance when capacitors are connected in :
- | |
|-------------|
| a) Parallel |
| b) Series. |
20. What is mutual inductance ? Explain the working of a transformer.



21. What is a high pass filter ? How is it designed ?
22. Explain zener action. How is a voltage regulator constructed using a zener diode ?
23. Explain the principle of working of an oscillator.
24. What are inverting amplifiers ? Explain its working using an op-amp.
25. What are binary numbers ? How is decimal to conversion done ?
26. Explain the working of an analog multimeter.

(W=4×2=8)

SECTION – D

Answer **any one** question.

27. Using circuit describe the construction and working of a full wave rectifier. What is the effect of an RC filter on the output voltage.
28. Explain the working of a digital to analog converter. Determine the resolution of a 6 bit DAC.

(W=1×4=4)