



Reg. No. : .....

Name : .....

**VI Semester B.Sc. Degree (CCSS – Reg./Supple./Improv.)  
Examination, May 2014  
CORE COURSE IN PHYSICS  
6B14 PHY : Digital Electronics**

Time : 3 Hours

Max. Weightage : 30

**Instructions :** Choose correct answer from Section A. Each bunch carries a wt. of 1.  
Answer any six from Sec. B. Each carries a wt. of 1.  
Answer any nine from Sec. C. Each carries a wt. of 2.  
Answer any one from Sec. D. Each carries a wt. of 4.

**SECTION – A**

Choose the correct answer. Each bunch carries a weightage of 1.

1. 1) The decimal equivalent of binary number 10101 is  
 a) 18                      b) 32                      c) 21                      d) 28
- 2) The 2's complement of 10011 is  
 a) 01100                  b) 01101                  c) 01111                  d) 1100
- 3) The ASCII code for character 'A' is  
 a) 4A                      b) 41                      c) 3A                      d) 33
- 4) The hexadecimal equivalent of octal 132 is  
 a) 3A                      b) 3B                      c) 5A                      d) 5C
2. 1)  $A.(\bar{A}+B) =$   
 a)  $\bar{A}B$                       b)  $A+B$                       c)  $\bar{A}+B$                       d)  $AB$
- 2) A four variable Boolean expression gives an output 1.  
 For  $A = 0, B = 1, C = 1$  and  $D = 0$ .  
 The Boolean equation is  
 a)  $A.B + C.D$                       b)  $(A + B)(C + D)$   
 c)  $(A.B.C)$                       d) None of these



3) A carrier of 100 V, 10 KHz is modulated by a 50 V, 1000 Hz sine wave.

The modulation factor is

- a) 50%                                      b) Over modulation  
c) 2%                                        d) 10%

4) As the modulation level is increased, the carrier power is

- a) Increased                                b) Decreased  
c) Remains the same                      d) Depends on the frequency of carrier

(2×1=2)

## SECTION – B

Answer **any six**. Each carries a wt. of 1.

(1 each)

3. Add + 5 and -7 in 2's complement binary.

4. Convert decimal 1449 to hexadecimal.

5. Write the Boolean equation and logic circuit of an EX-OR gate.

6. Apply De Morgans principle to simplify the boolean equation  $\overline{AB + C}$ .

7. Sketch the circuit of a half adder.

8. What do you mean by over modulation ?

9. Draw the frequency spectrum of an amplitude modulated wave.

10. What is meant by demodulation ?

(6×1=6)

## SECTION – C

Answer **any nine**. Each carries a wt. of 2.

(2 each)

11. Perform the following arithmetic operations on signed binary numbers.

- a) Add + 39 and -22.  
b) Subtract -21 from +39.

12. Explain De Morgan's theorems.

13. Simplify the following Boolean equations.

- a)  $(\bar{A} + B)(A + B)$   
b)  $ABC + A\bar{B}C + AB\bar{C}$ .



14. Realise the logic expression  $Y = (A + B)(\bar{A} + C)(B + D)$  using basic gates.

15. Show the realisation of OR gate and AND gate using NAND gates.

16. Draw a truth table for the Boolean equation  $Y = (A + B)C$ .

17. Show the implementation of a 4 bit parallel adder using full adders.

18. Sketch the block diagram of an amplitude modulator.

19. What is the need for modulation in communication system ?

20. An audio signal of 1 KHz is used to modulate a carrier of 500 KHz. Determine the side bands and band width.

21. Explain any two advantages of frequency modulation over amplitude modulation.

22. What do you mean by pulse modulation ?

(9×2=18)

## SECTION – D

Answer **any one**. Each carries a wt. of 4.

(4 each)

23. A three input digital circuit gives a high output for the following input logic

| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Draw a K-map for the truth table and obtain a minimised Boolean expression.

24. With the help of necessary diagrams, explain the demodulation of an amplitude modulated signal.

(1×4=4)